
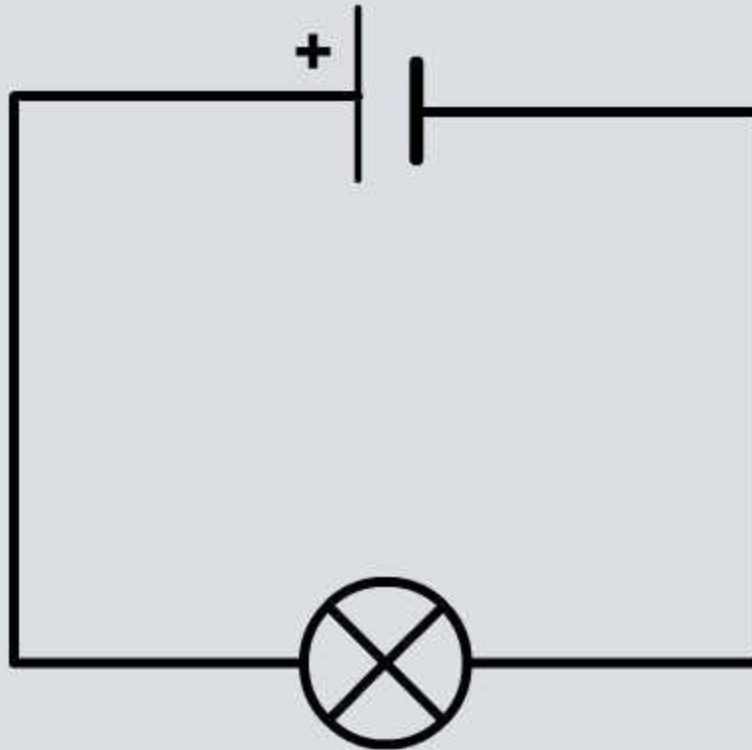


Series Circuits

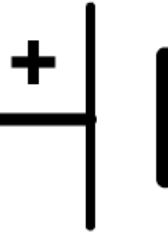


What is a series circuit?



This is a simple **series** circuit.


In a simple series circuit, everything is **connected in one loop** across the terminals of the battery. There are no points where the current can split or join (these are called junctions).

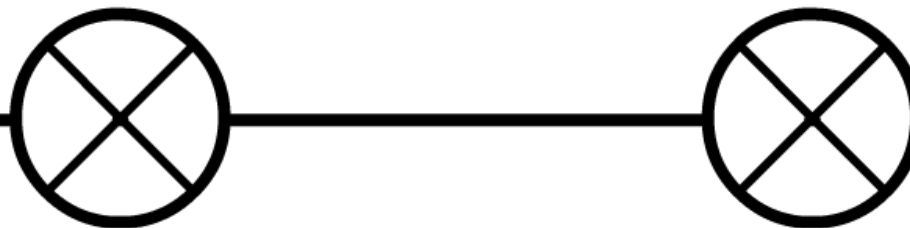This circuit has two lamps connected in series. Circuits are always drawn using straight lines.




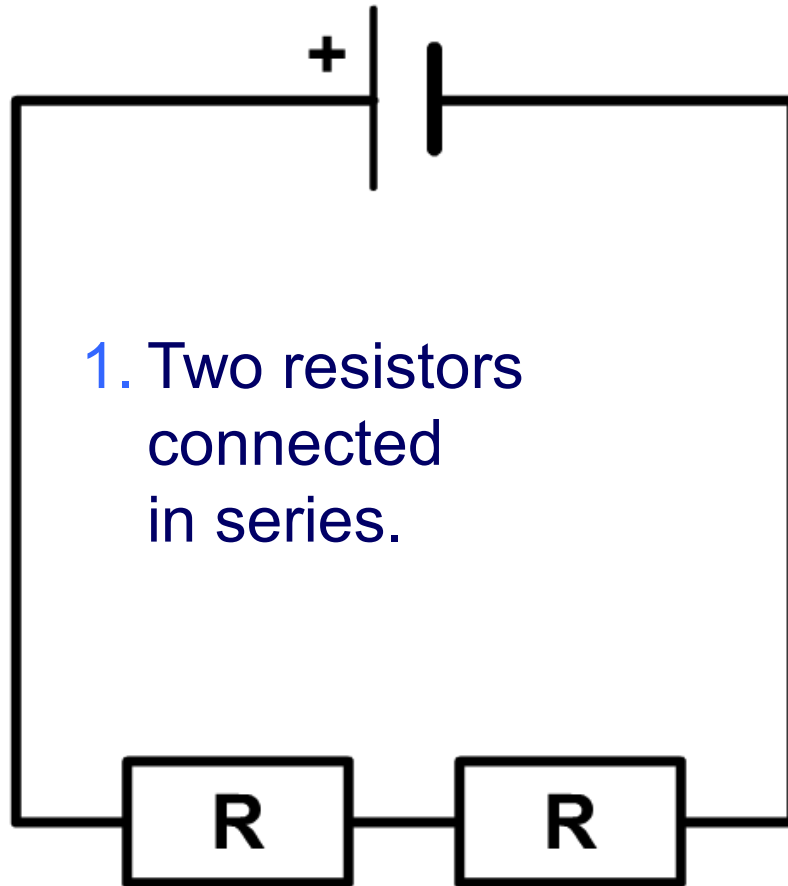Examples of series circuits

Here are some other simple series circuits:



1. Two resistors connected in series.

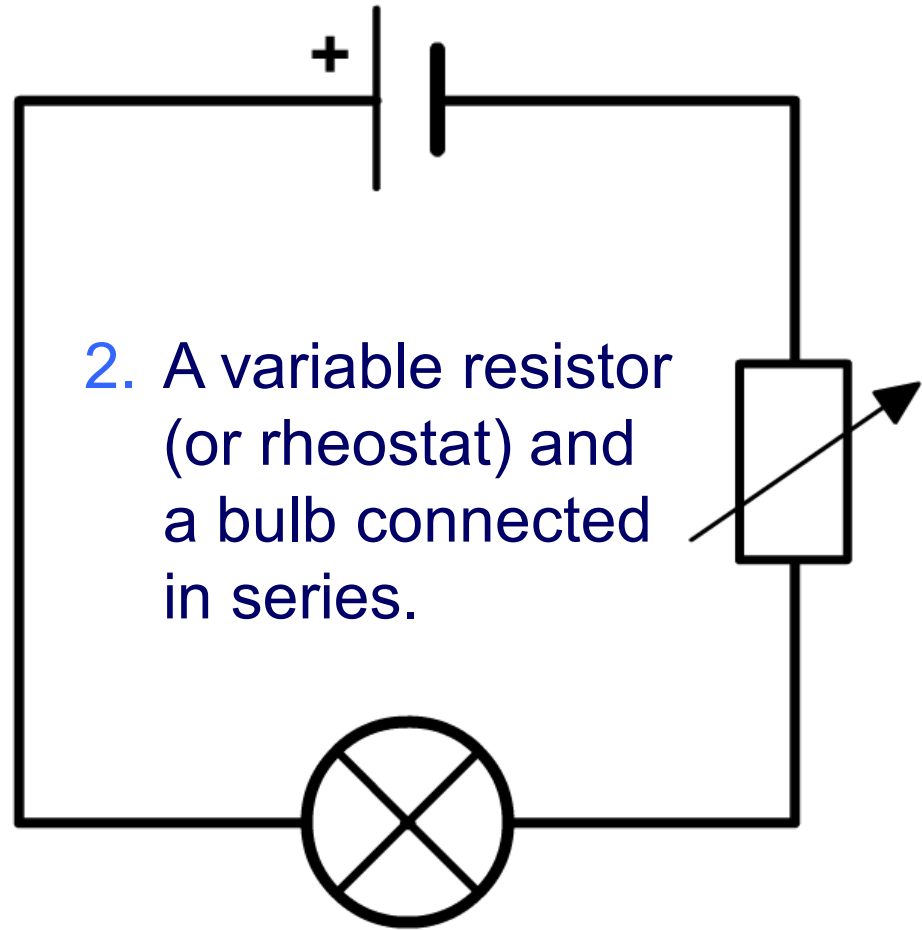

2. A variable resistor (or rheostat) and a bulb connected in series.




Measuring current

The unit of measurement for **current** is the **amp**, which has the symbol A.

Current is measured using a device called an **ammeter**.

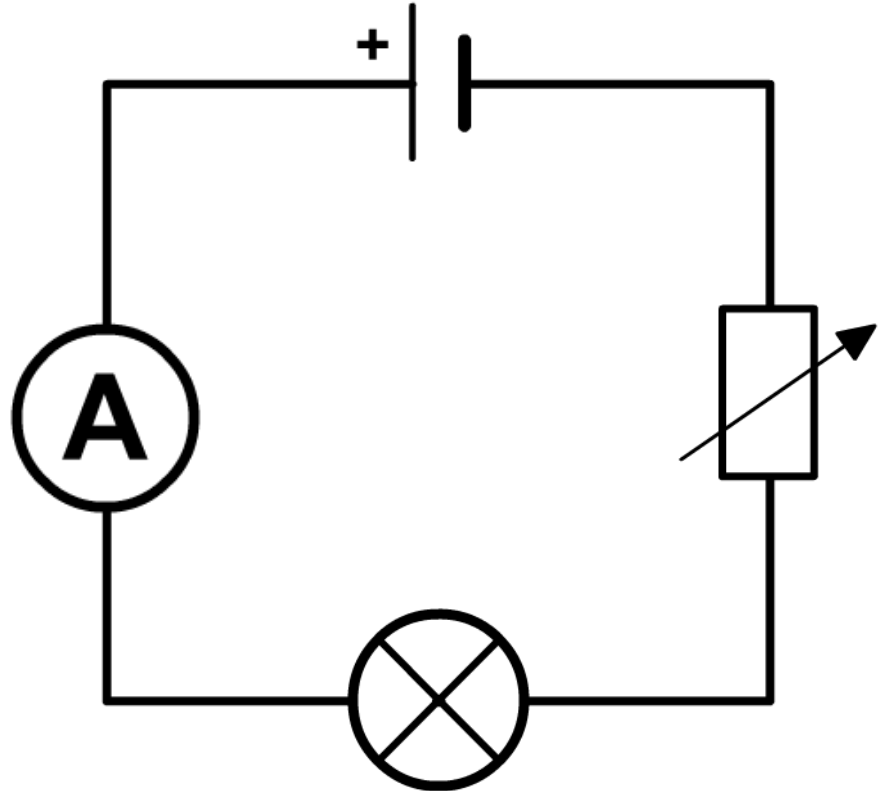In a circuit diagram, an ammeter is shown by an 'A' in a circle.




When measuring the current through a component, the ammeter is always connected in **series** (in the same loop) with that component.



How can we investigate current in a series circuit?

How can we investigate how components in a series circuit affect the current?



Click "**start**" to find out.

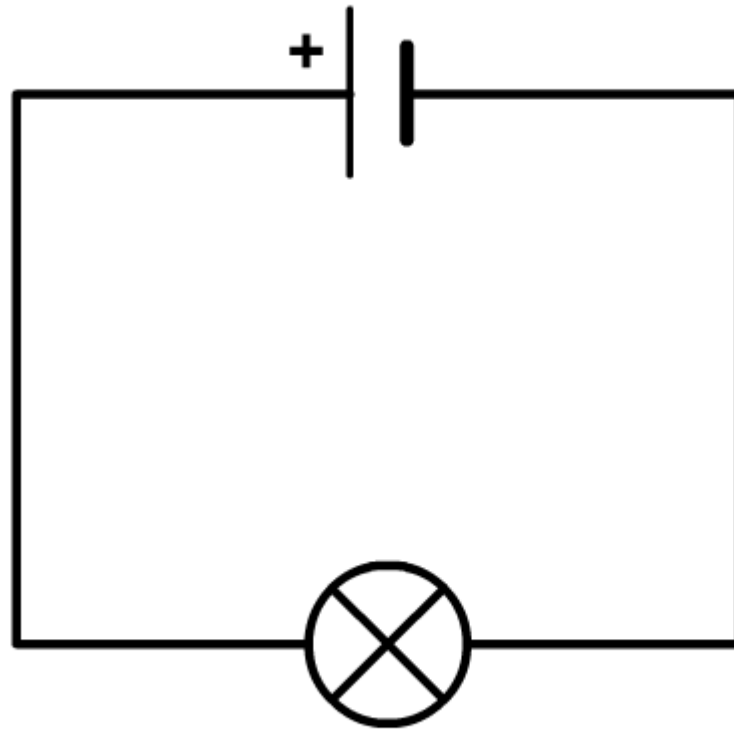

start



What are the missing words about series circuits?

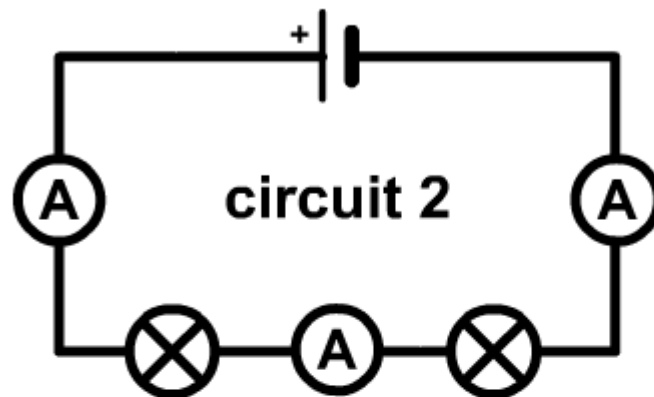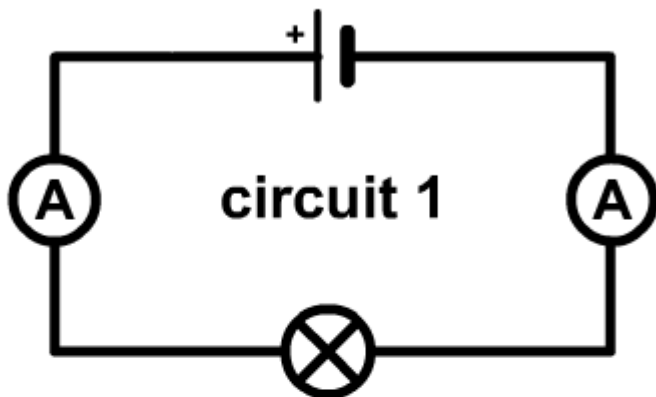

Circuit 1:

1a. The current at different positions in the circuit, before and after the bulb, was .

1b. Therefore current used up by the components in the circuit.



solve




Voltage is measured using a device called a voltmeter. In a circuit diagram, a voltmeter is given the symbol V.

When measuring the voltage across a component, the voltmeter is always connected in **parallel** with (or across) the component.

This is still a series circuit, as the voltmeter does not affect the circuit.

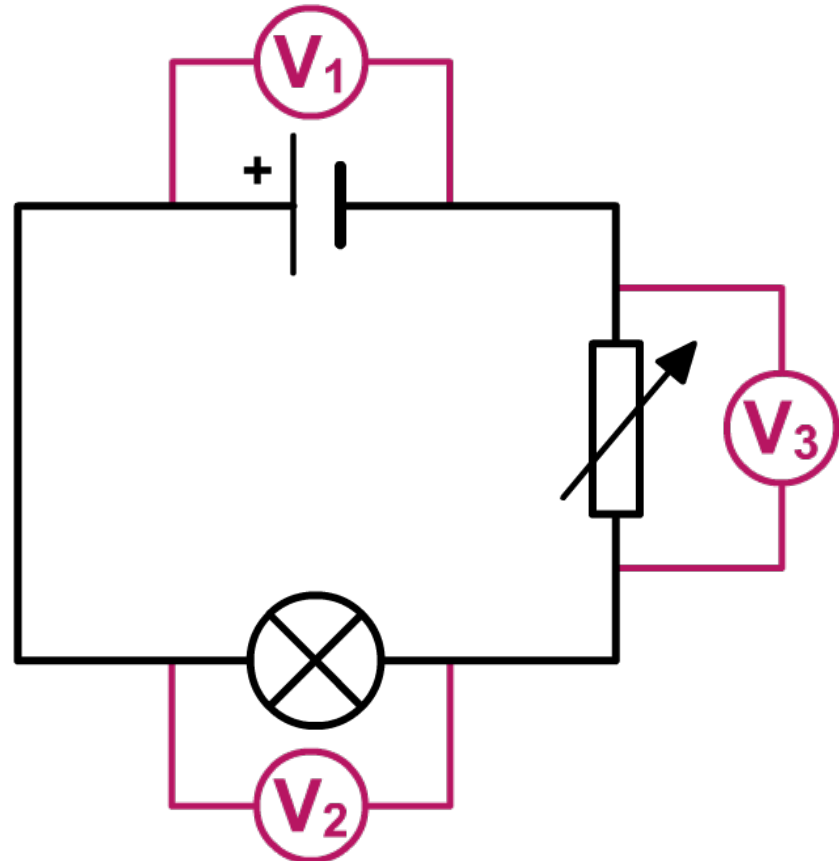
The voltage supplied by the battery is **shared** between all the components in a series circuit.



How can we investigate voltage in a series circuit?

How can we investigate how components in a series circuit affect the voltage?


Click "**start**" to find out.

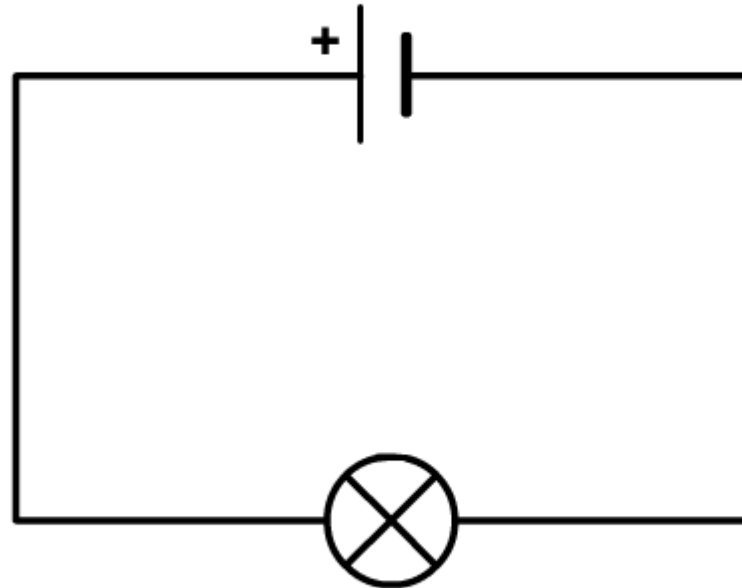

start



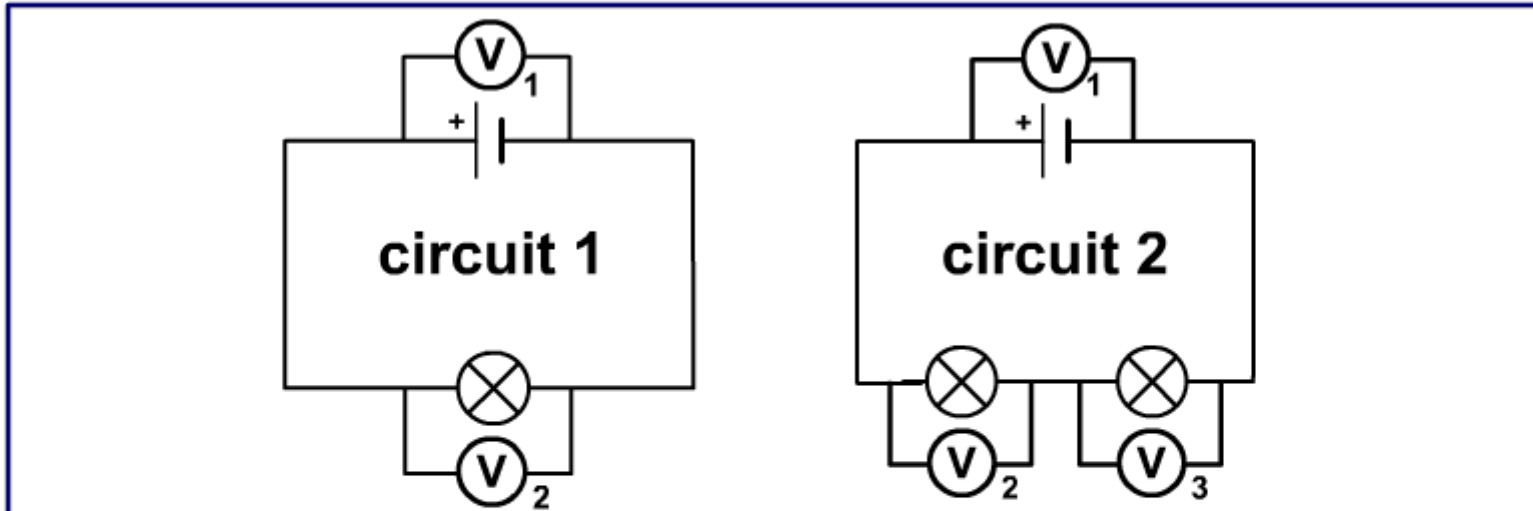What are the missing words about voltage in series circuits?



1a. The current is the of electricity around the circuit.

1b. The is the amount of push.



solve



Current or voltage?

Does each statement apply to current or voltage?

current

voltage

measured using
a voltmeter

?

C


solve

↶

How can we investigate cells in a series circuit?

How can we investigate how changing the number of cells affects a series circuit?


Click "**start**" to find out.

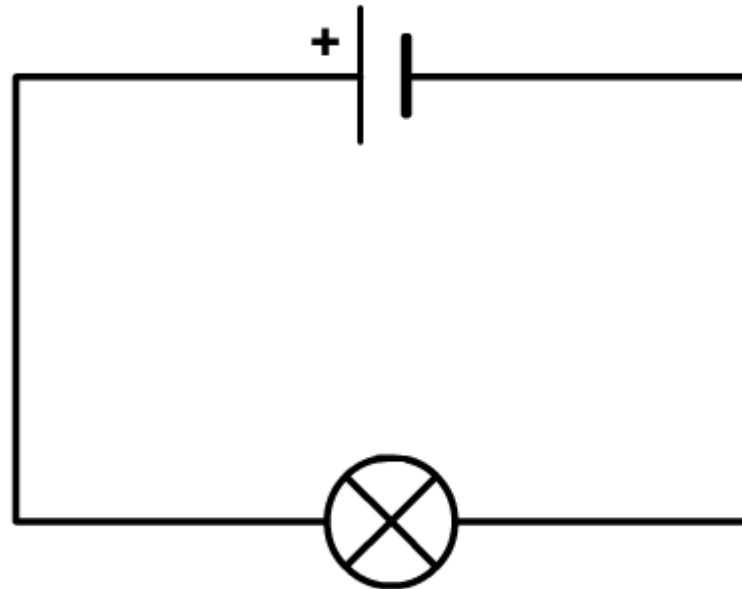

start



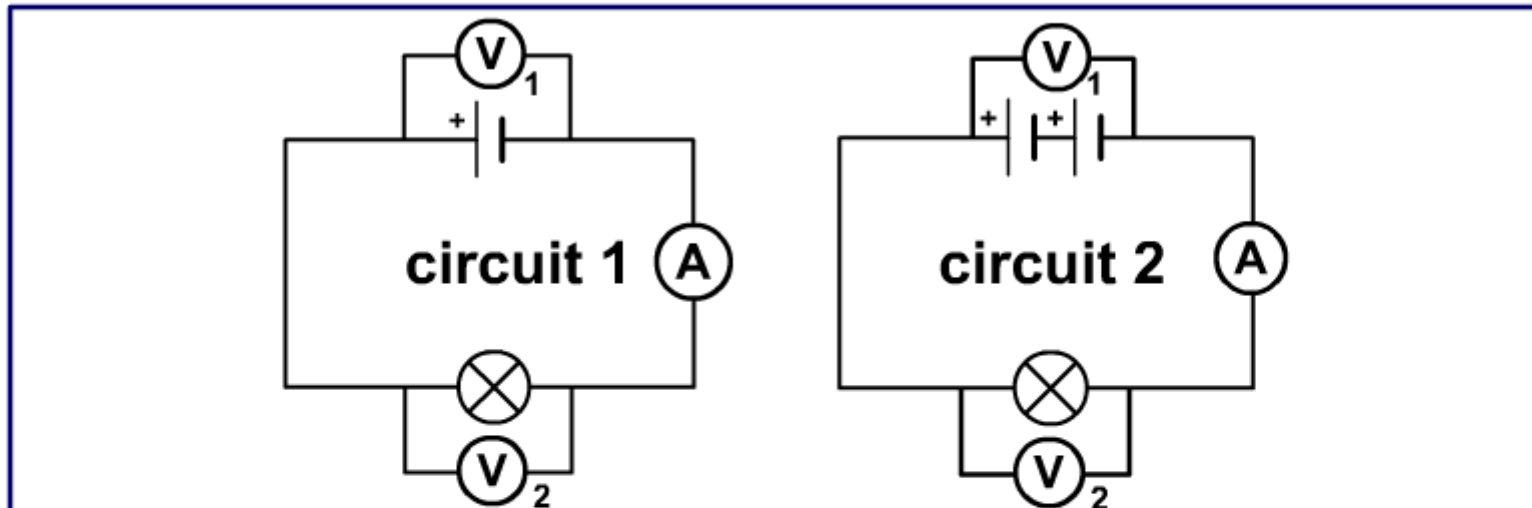What are the missing words about cells in series circuits?



1a. Increasing the number of cells the current that flows in the circuit.

1b. The flowing in the circuit depends on the of the power supply.



solve




Series circuits – key ideas

1. In a **series circuit** the current is the **same** in all parts of the circuit. Series circuits are found in flashlights and strings of Christmas lights.
2. The supply voltage is **shared** between the components in a series circuit. (The sum of the voltage across each component is the same as the total supply voltage.)
3. The current depends on the voltage in any circuit.




Make your own series circuit


Investigating series circuits

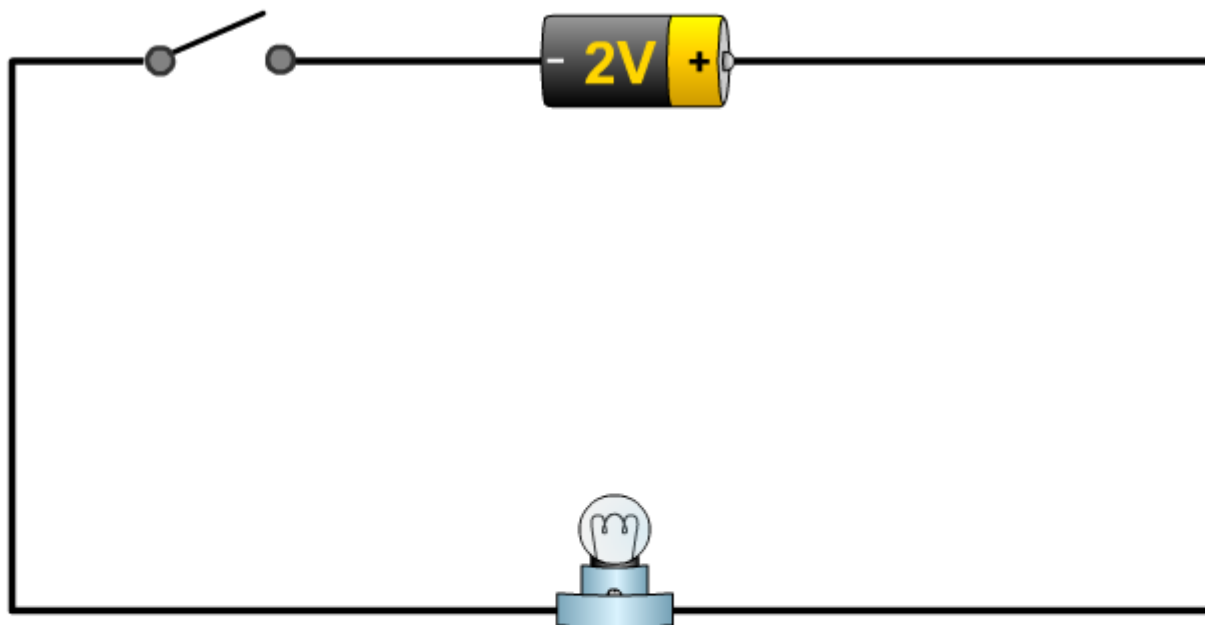

cells

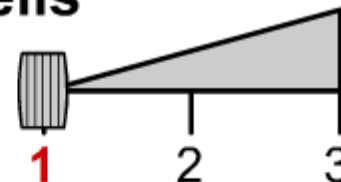

bulbs

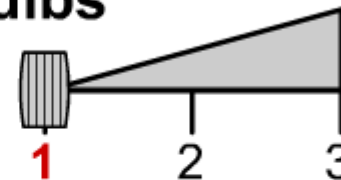

Are these statements about series circuits true or false?

1.	Current is used up in a series circuit.	
2.	Ammeters are connected in series.	
3.	Voltmeters are connected in series.	
4.	Current varies around a series circuit if there are several components.	
5.	Supply voltage is shared between the components in a series circuit.	
6.	Increasing the number of cells increases both the voltage and current in a series circuit.	

true

false



solve

